Homework #2

7112056080 鍾期安

1.

(a)

Input and espresso result ignore the don't-care

```
ouo@ouo-virtual-machine:~/文件$ nano BCD-to-seven.pla
 GNU nano 6.2
                                                         BCD-to-seven.pla
.i 4
.0 2
.ilb ABCD
.ob e f
.p 16
0000 11
0001 00
0010 10
0011 00
0100 01
0101 01
0110 11
0111 00
1000 11
1001 01
1010 00
1011 00
1100 00
1101 00
1110 00
1111 00
```

ouo@ouo-virtual-machine:~/文件\$ espresso BCD-to-seven.pla > output.pla ouo@ouo-virtual-machine:~/文件\$ nano output.pla

```
GNU nano 6.2

.i 4

.o 2

.ilb A B C D

.ob e f

.p 5

01-0 01

0-10 10

100- 01

-000 11


.e
```

```
ouo@ouo-virtual-machine:~/文件$ nano BCD-to-seven-DC.pla
```

```
GNU nano 6.2
                                                          BCD-to-seven-DC.pla
.i 4
.0 2
.ilb ABCD
.ob e f
.р 16
0000 11
0001 00
0010 10
0011 00
0100 01
0101 01
0110 11
0111 00
1000 11
1001 01
1010 --
1011 --
1100 --
1101 --
1110 --
1111 --
ouo@ouo-virtual-machine:~/文件$ espresso BCD-to-seven-DC.pla > output.pla
ouo@ouo-virtual-machine:~/文件$ nano output.pla
 GNU nano 6.2
                                                                  output.pla
.i 4
.0 2
.ilb A B C D
.ob e f
.р 5
-1-0 01
--10 10
-000 11
1--- 01
-10- 01
.e
```


(b) 可以,

e 的卡諾圖:

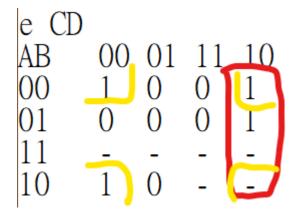


簡化結果:CD'+B'D' espresso: CD'+B'C'D'

f 的卡諾圖:

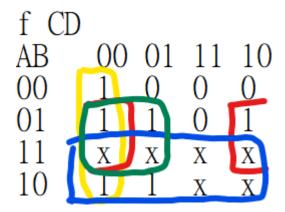

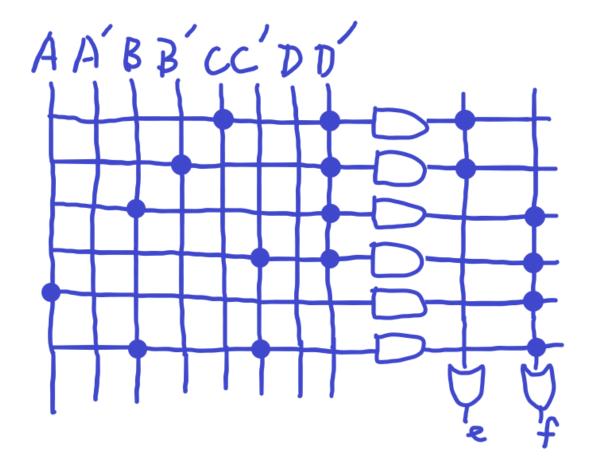簡化結果:BD'+C'D'+A+BC' espresso: BD'+B'C'D'+A+BC'



(1) no option

```
real 0m0.161s
user 0m0.149s
sys 0m0.010s
```

(2) QM algorithm

```
real 0m1.367s
user 0m1.354s
sys 0m0.007s
```

Machine: Ubuntu 22.04.3 LTS (VMware)